

# **Induction Motor**

# Induction Motors

- **The single-phase induction motor is the most frequently used motor in the world**
- **Most appliances, such as washing machines and refrigerators, use a single-phase induction machine**
- **Highly reliable and economical**

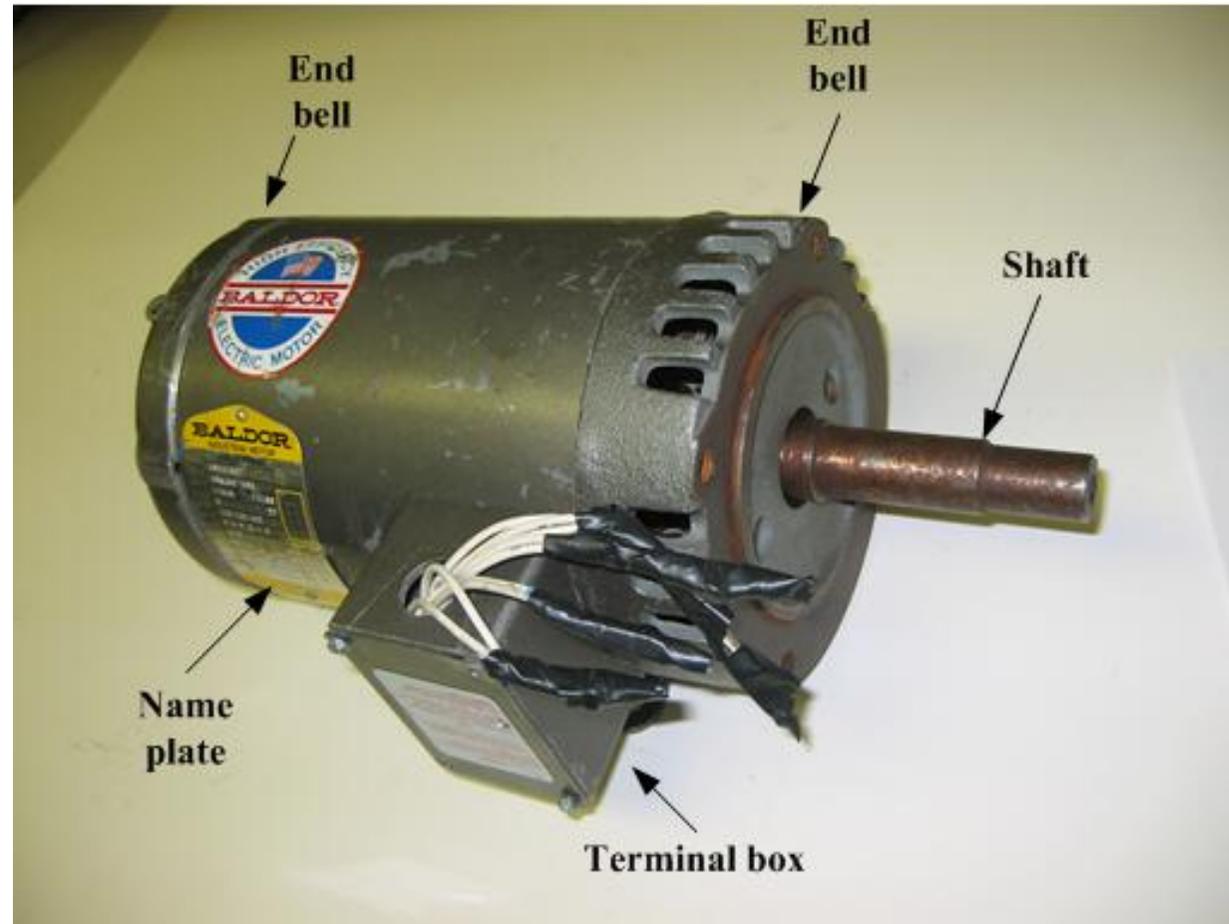


Figure 1 Single-phase induction motor.


# Induction Motors

- **For industrial applications, the three-phase induction motor is used to drive machines**
- **Figure 2 Large three-phase induction motor. (Courtesy Siemens).**



# Induction Motors

**Figure 3**  
**Induction motor**  
**components.**

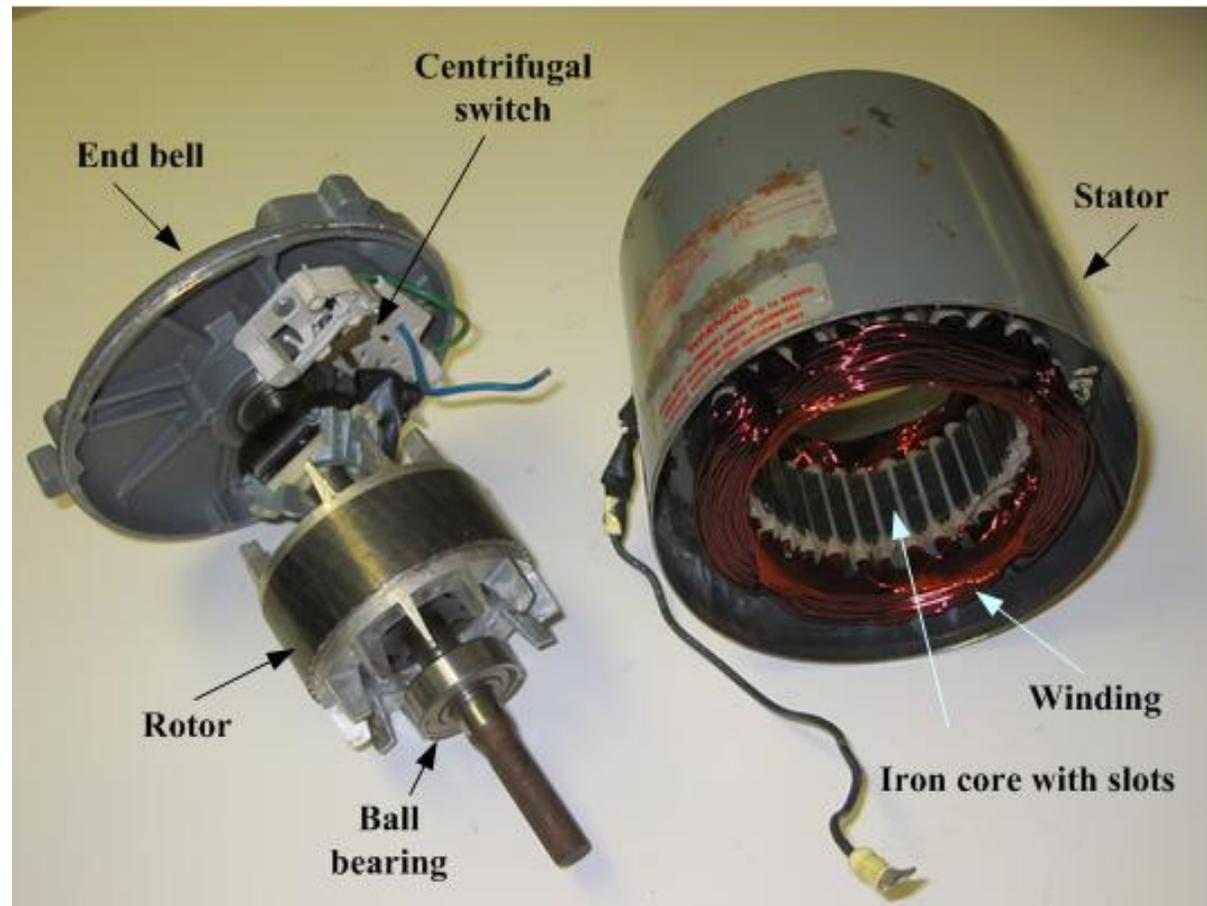


# Induction Motors

- **The motor housing consists of three parts:**
  - **The cylindrical middle piece that holds the stator iron core,**
  - **The two bell-shaped end covers holding the ball bearings.**
  - **This motor housing is made of cast aluminum or cast iron. Long screws hold the three parts together.**
  - **The legs at the middle section permit the attachment of the motor to a base.**
  - **A cooling fan is attached to the shaft at the left-hand side. This fan blows air over the ribbed stator frame.**


# Induction Motors

**Figure 4 Stator  
of a large  
induction  
motor.  
(Courtesy  
Siemens).**

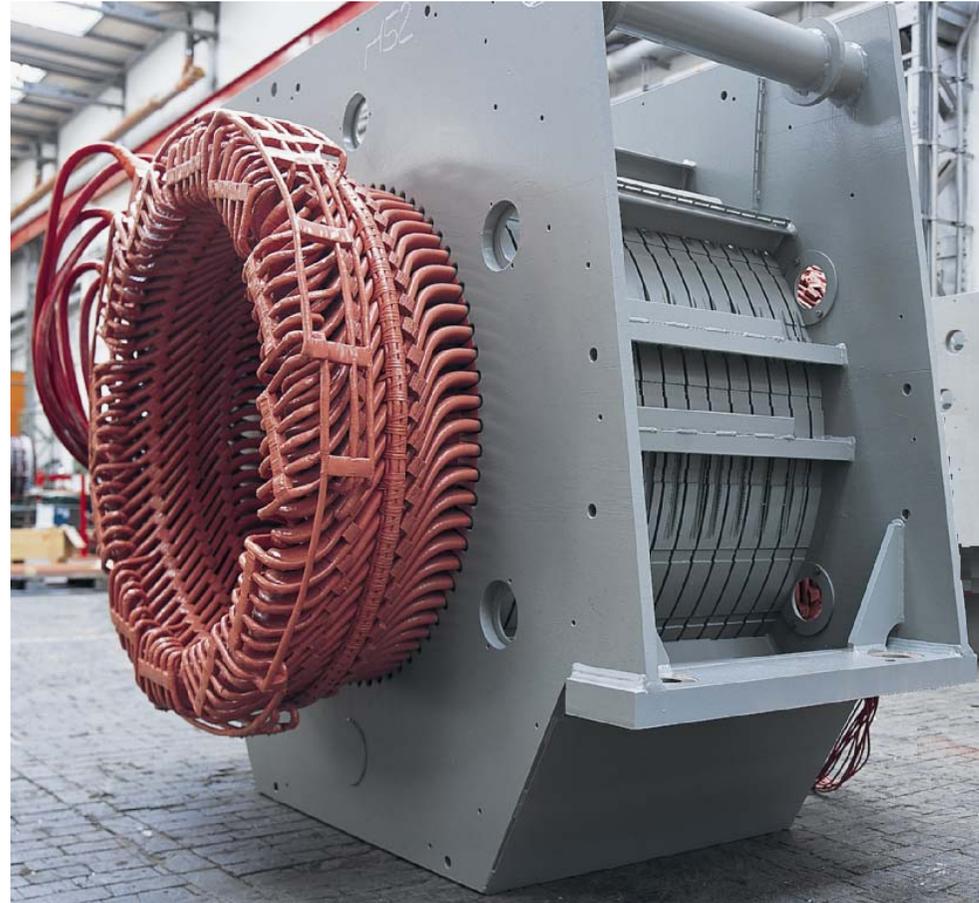

# Induction Motors


- The iron core has cylindrical shape and is laminated with slots
- The iron core on the figure has paper liner insulation placed in some of the slots.
- In a three-phase motor, the three phase windings are placed in the slots
- A single-phase motor has two windings: the main and the starting windings.
- Typically, thin enamel insulated wires are used

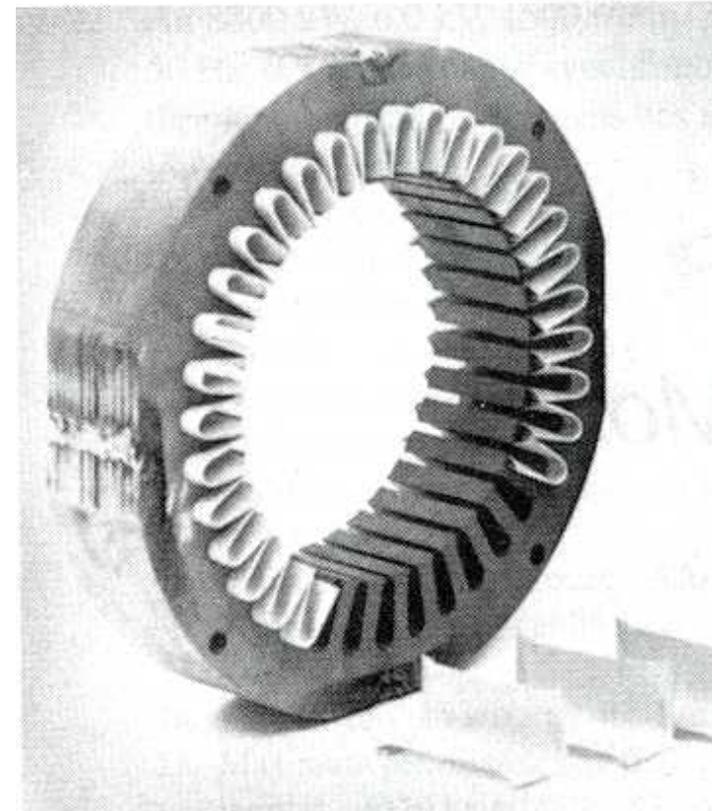

**Figure 5 Stator iron core without windings**

# Induction Motors

- A single-phase motor has two windings: the main and the starting windings
- The elements of the laminated iron core are punched from a silicon iron sheet.
- The sheet has 36 slots and 4 holes for the assembly of the iron core.

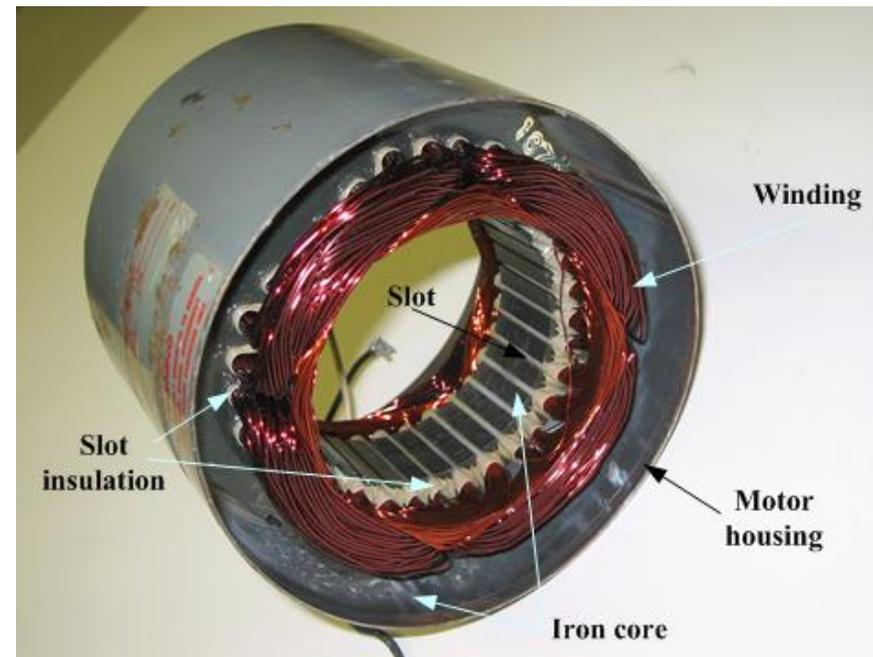

**Figure 6** Single-phase stator with main windings.

# Induction Motors

- The elements of the laminated iron core are punched from a silicon iron sheet.
- The sheet has 36 slots and 4 holes for the assembly of the iron core


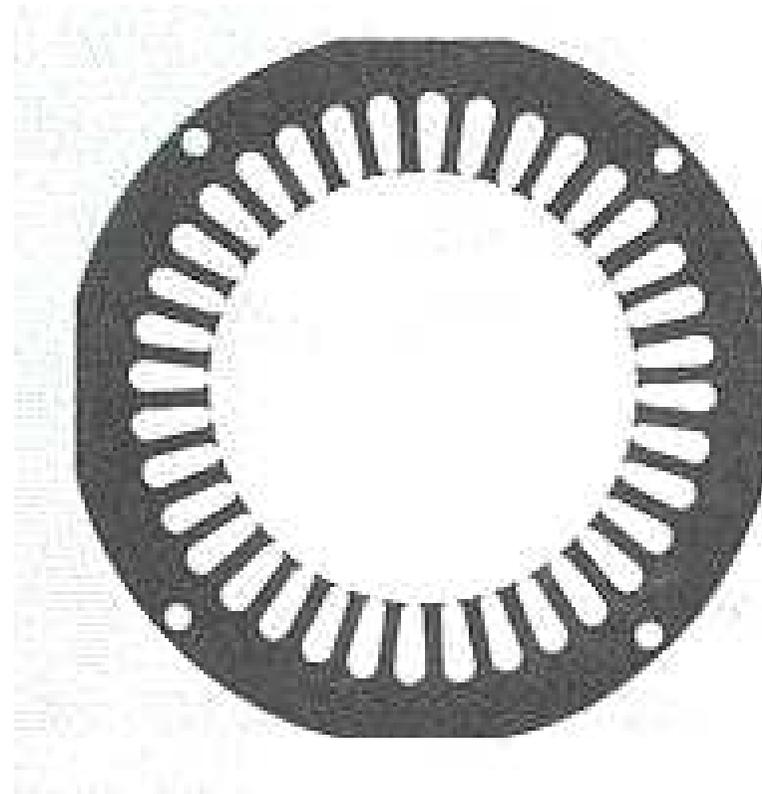


Figure 7 Stator iron core sheet.

# Induction Motors

Figure 8 Stator and rotor magnetic circuit

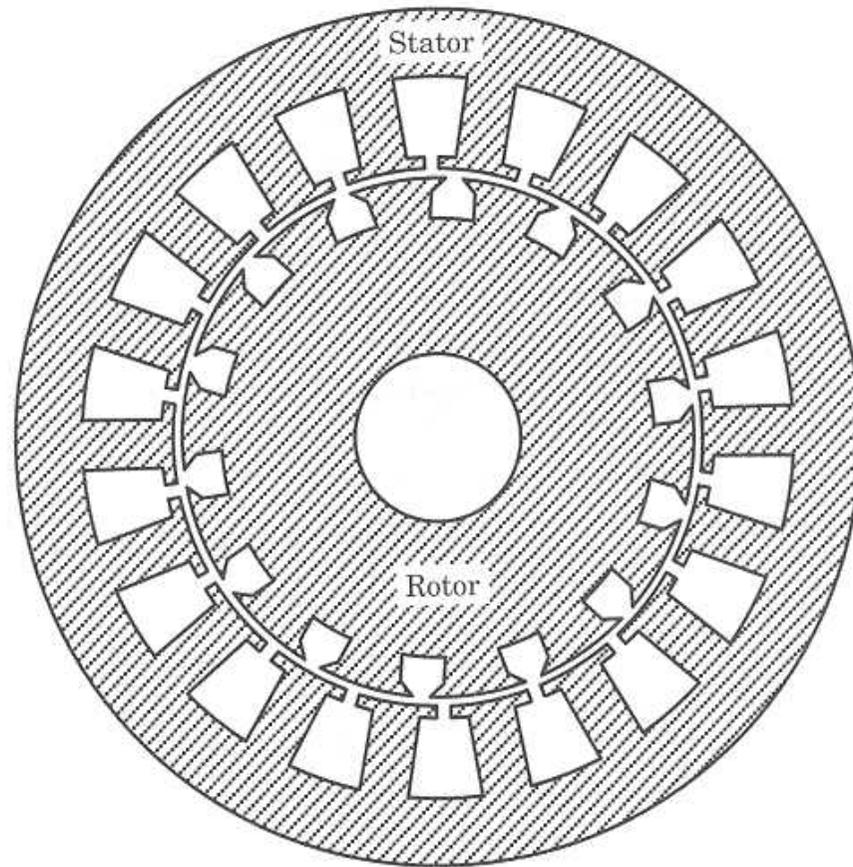


# Induction Motors

## Squirrel cage rotor.


- This rotor has a laminated iron core with slots, and is mounted on a shaft.
- Aluminum bars are molded in the slots and the bars are short circuited with two end rings.
- The bars are slanted on a small rotor to reduce audible noise.
- Fins are placed on the ring that shorts the bars. These fins work as a fan and improve cooling.

# Induction Motors

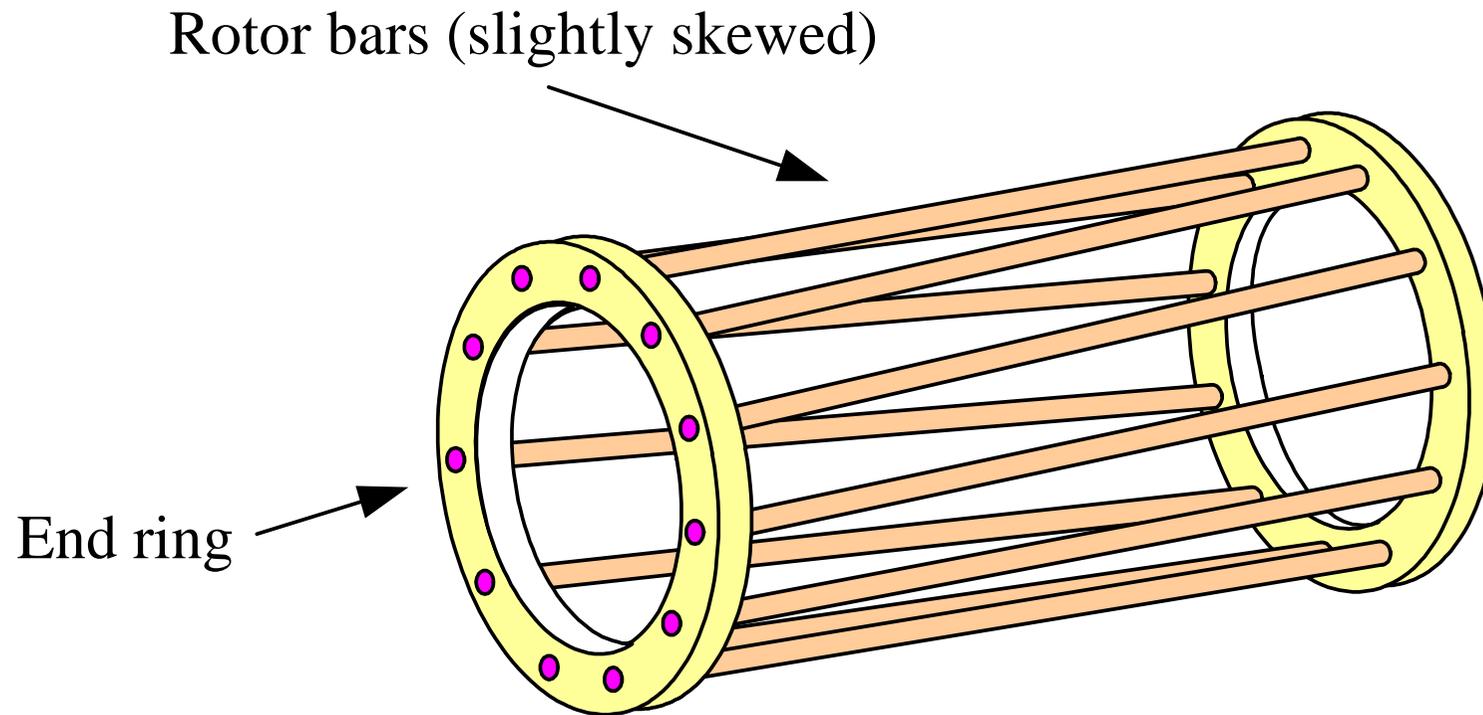

**Figure 9 Squirrel cage rotor concept.**

# Induction Motors

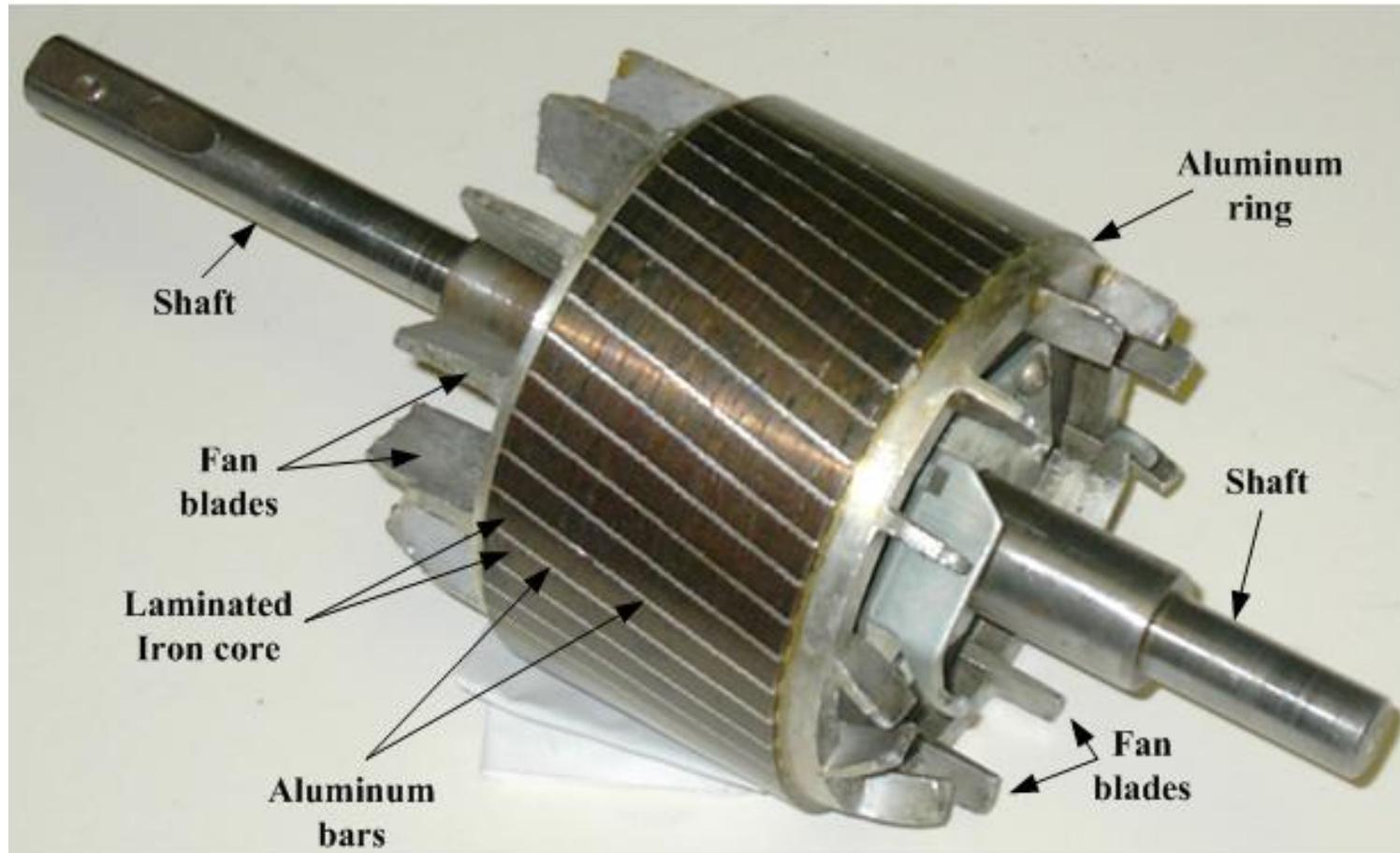


**Figure 10 Squirrel cage rotor.**

# Induction Motors

## **Wound rotor.**

- Most motors use the squirrel-cage rotor because of the robust and maintenance-free construction.
- However, large, older motors use a wound rotor with three phase windings placed in the rotor slots.
- The windings are connected in a three-wire wye.
- The ends of the windings are connected to three slip rings.
- Resistors or power supplies are connected to the slip rings through brushes for reduction of starting current and speed control

# Induction Motors

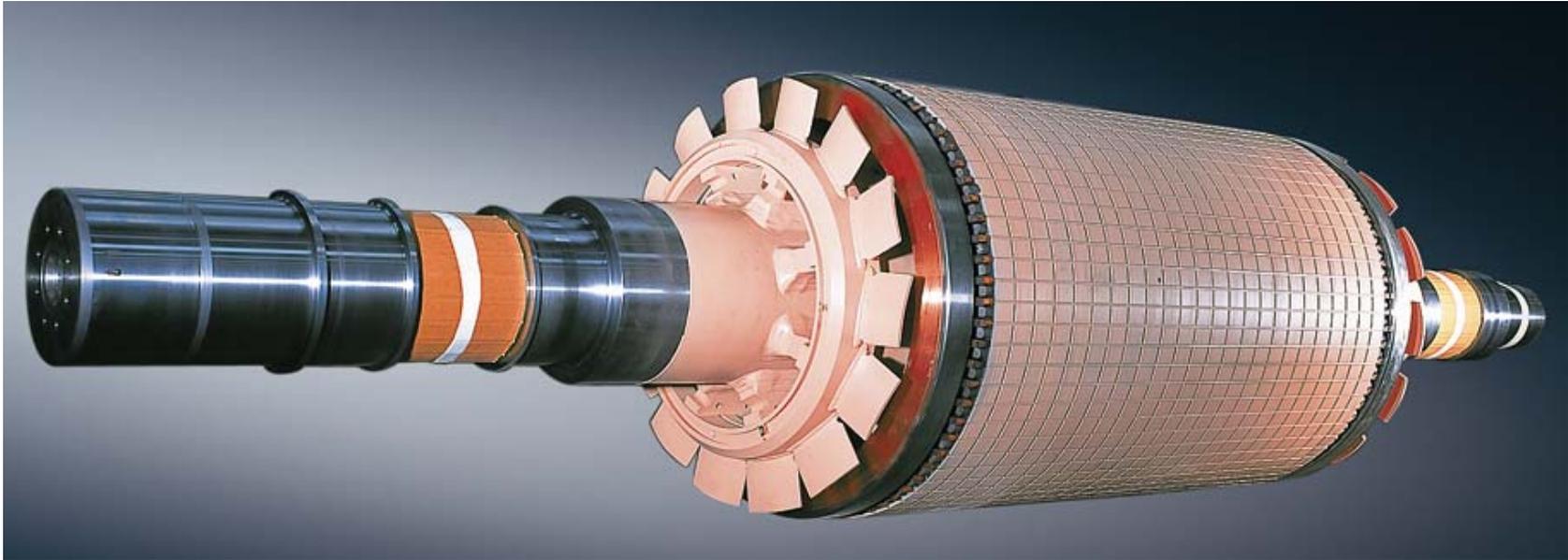

**Figure 11 Rotor of a large induction motor. (Courtesy Siemens).**

# **Operating principle**

# Induction Motors

- This two-pole motor has three stator phase windings, connected in three-wire wye.
- Each phase has  $2 \times 3 = 6$  slots. The phases are shifted by  $120^\circ$
- The squirrel cage rotor has short-circuited bars.
- The motor is supplied by balanced three-phase voltage at the terminals.
- The stator three-phase windings can also be connected in a delta configuration.

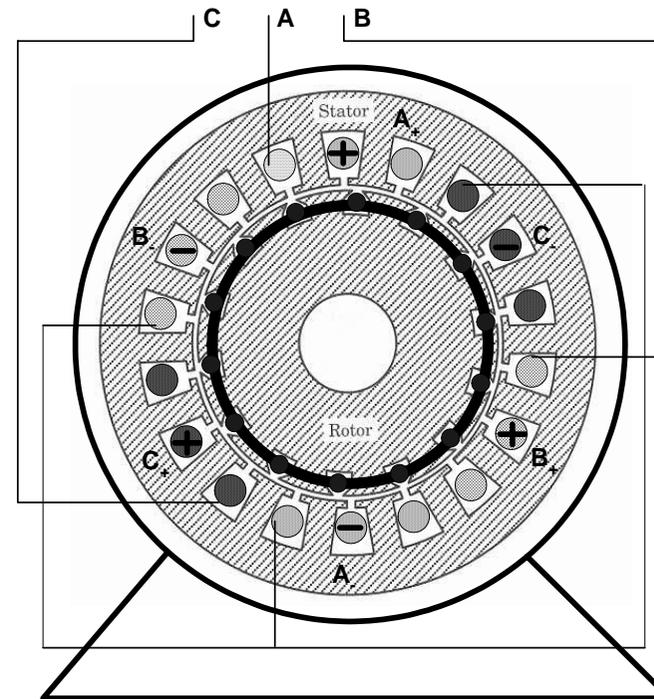


Figure 11 Connection diagram of a two-pole induction motor with squirrel cage rotor.

# Induction Motors

## Operation Principle

- **The three-phase stator is supplied by balanced three-phase voltage that drives an ac magnetizing current through each phase winding.**
- **The magnetizing current in each phase generates a pulsating ac flux.**
- **The flux amplitude varies sinusoidally and the direction of the flux is perpendicular to the phase winding.**

# Induction Motors

## Operation Principle

- **The three-phase stator is supplied by balanced three-phase voltage that drives an ac magnetizing current through each phase winding.**
- **The magnetizing current in each phase generates a pulsating ac flux.**
- **The total flux in the machine is the sum of the three fluxes.**
- **The summation of the three ac fluxes results in a rotating flux, which turns with constant speed and has constant amplitude.**


# Induction Motors

## Operation Principle

- **The rotating flux induces a voltage in the short-circuited bars of the rotor. This voltage drives current through the bars.**
- **The induced voltage is proportional with the difference of motor and synchronous speed. Consequently the motor speed is less than the synchronous speed**
- **The interaction of the rotating flux and the rotor current generates a force that drives the motor.**
- **The force is proportional with the flux density and the rotor bar current**

# Induction Motors

- The figure shows the three components of the magnetic field at a phase angle of  $-60^\circ$ .
- Each phase generates a magnetic field vector.
- The vector sum of the component vectors  $\Phi_a$ ,  $\Phi_b$ ,  $\Phi_c$  gives the resulting rotating field vector  $\Phi_{rot}$ .
- The amplitude is 1.5 times the individual phase vector amplitudes, and  $\Phi_{rot}$  rotates with constant speed.

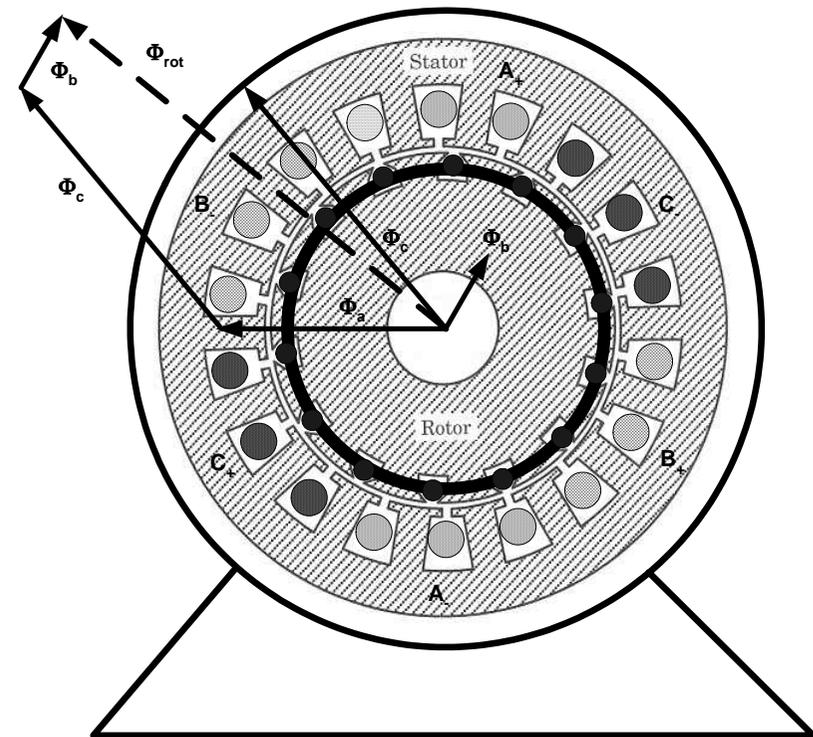


**Figure 12 Three-phase winding-generated rotating magnetic field.**

# Induced Voltage Generation

# Induction Motors

## Faraday's law


- **Voltage is induced in a conductor that moves perpendicular to a magnetic field,**
- **The induced voltage is:**

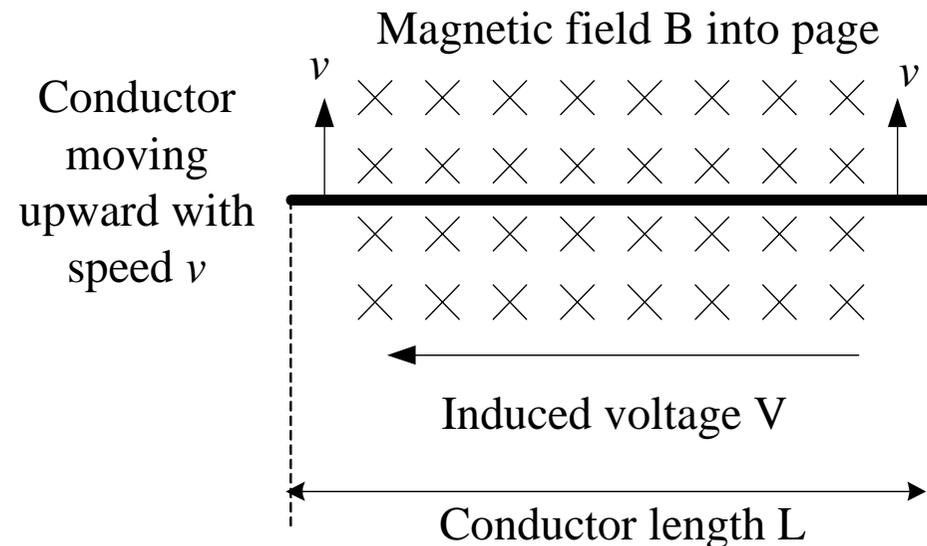

**Figure 14 Voltage induced in a conductor moving through a magnetic field.**
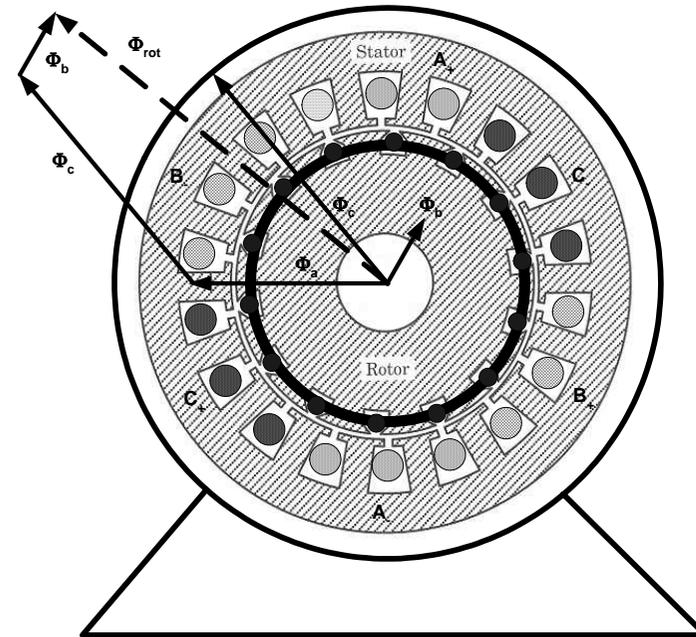
# Induction Motors


- The three-phase winding on the stator generates a rotating field.
- The rotor bar cuts the magnetic field lines as the field rotates.
- The rotating field induces a voltage in the short-circuited rotor bars
- The induced voltage is proportional to the speed difference between the rotating field and the spinning rotor



$$V = B L (v_{\text{syn}} - v_{\text{m}})$$
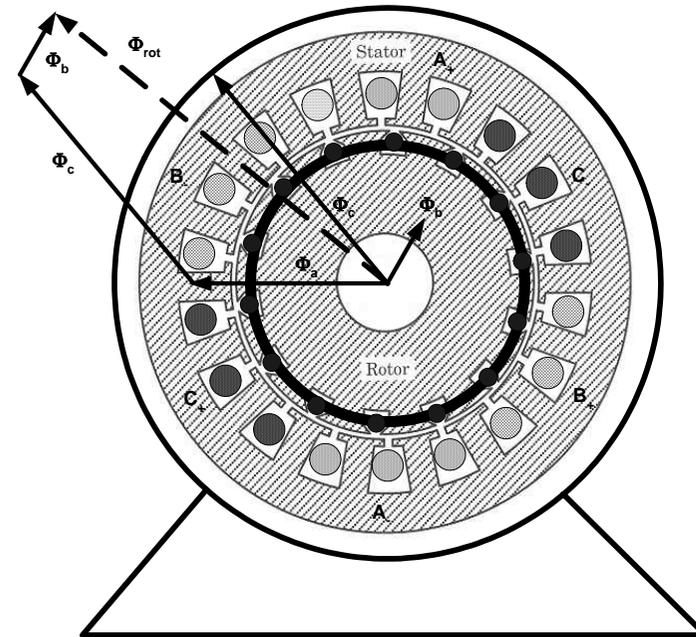
# Induction Motors

- The speed of flux cutting is the difference between the magnetic field speed and the rotor speed.
- The two speeds can be calculated by using the radius at the rotor bar location and the rotational speed.



$$v_{syn} = 2\pi r_{rot} n_{syn}$$

$$v_{mot} = 2\pi r_{rot} n_m$$

$$V_{bar} = 2\pi r_{rot} \mathbf{B} \ell_{rot} (n_{syn} - n_m)$$

# Induction Motors

- **The voltage and current generation in the rotor bar require a speed difference between the rotating field and the rotor.**
- **Consequently, the rotor speed is always less than the magnetic field speed.**
- **The relative speed difference is the *slip*, which is calculated using**

$$S = \frac{n_{sy} - n_m}{n_{sy}} = \frac{\omega_{sy} - \omega_m}{\omega_{sy}}$$

**The synchronous speed is**

$$n_{sy} = \frac{f}{p/2}$$

# **Motor Force Generation**

# Induction Motors

- The interaction between the magnetic field  $B$  and the current generates a force

$$\mathbf{F} = \mathbf{B} \mathbf{L} \mathbf{I}$$


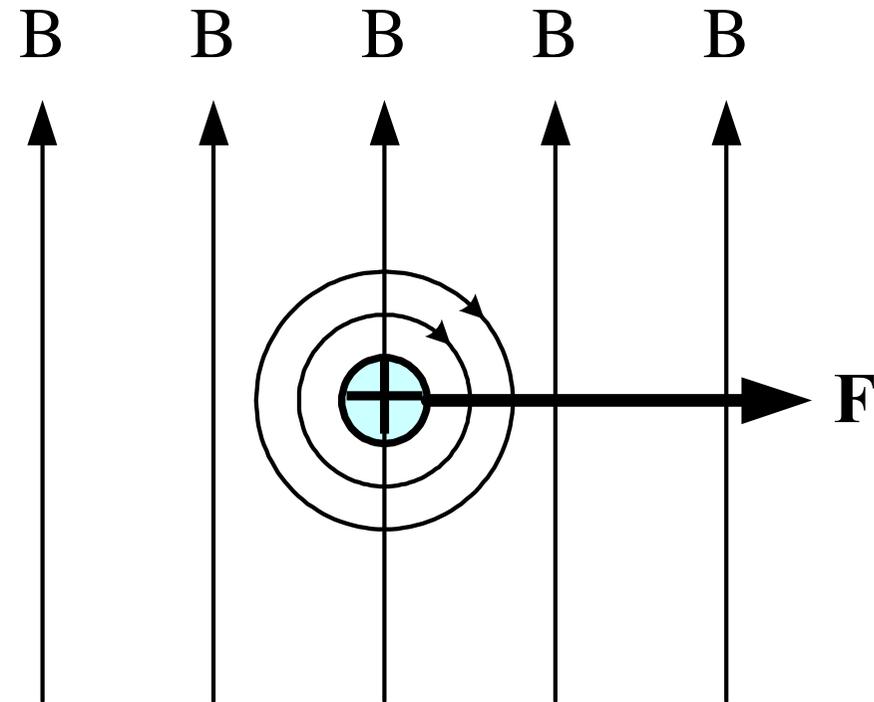


Figure 15 Force direction on a current-carrying conductor placed in a magnetic field ( $B$ ) (current into the page).

# Induction Motors

## Force generation in a motor

- **The three-phase winding generates a rotating field;**
- **The rotating field induces a current in the rotor bars;**
- **The current generation requires a speed difference between the rotor and the magnetic field;**
- **The interaction between the field and the current produces the driving force.**

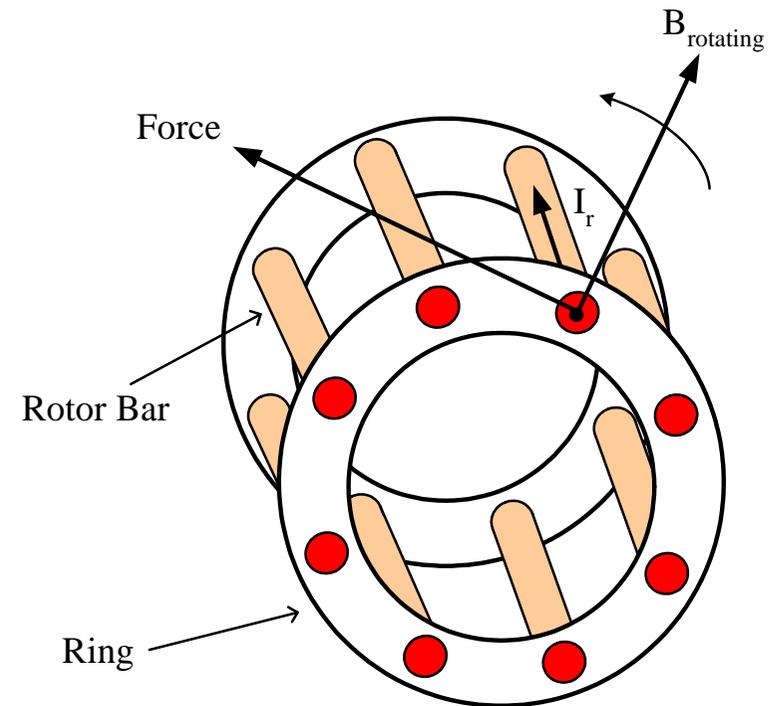

**Figure 16 Rotating magnetic field generated driving force.**

# Equivalent circuit


# Induction Motors

- An induction motor has two magnetically coupled circuits: the stator and the rotor. The latter is short-circuited.
- This is similar to a transformer, whose secondary is rotating and short-circuited.
- The motor has balanced three-phase circuits; consequently, the single-phase representation is sufficient.
- Both the stator and rotor have windings, which have resistance and leakage inductance.
- The stator and rotor winding are represented by a resistance and leakage reactance connected in series

# Induction Motors

- **A transformer represents the magnetic coupling between the two circuits.**
- **The stator produces a rotating magnetic field that induces voltage in both windings.**
  - **A magnetizing reactance ( $X_m$ ) and a resistance connected in parallel represent the magnetic field generation.**
  - **The resistance ( $R_c$ ) represents the eddy current and hysteresis losses in the iron core**
- **The induced voltage is depend on the slip and the turn ratio**

# Induction Motors

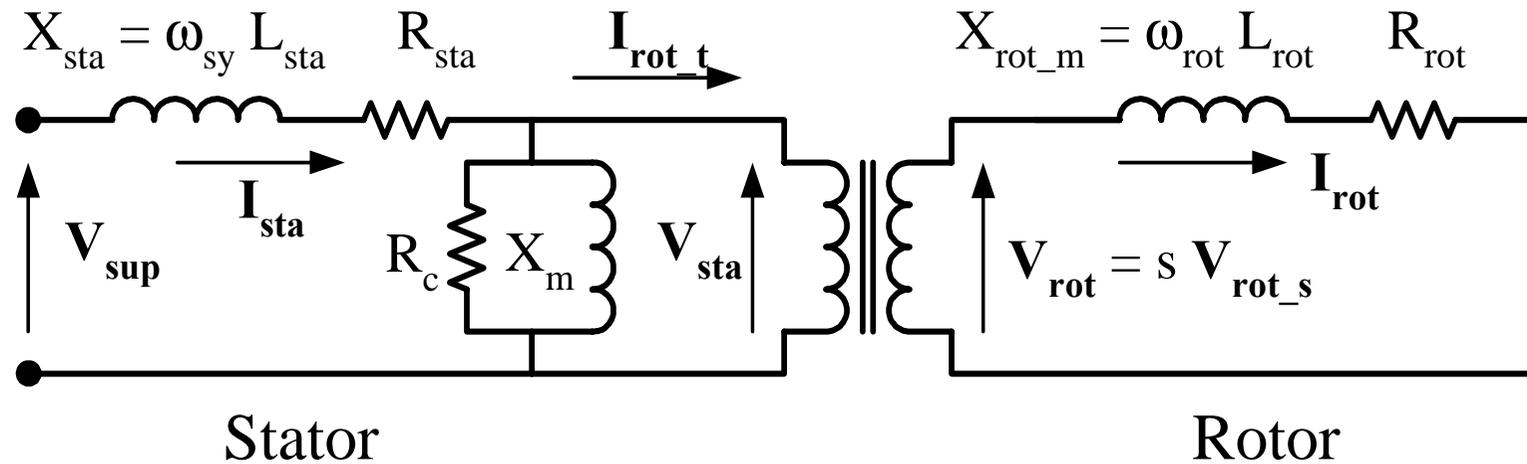

**Figure 17 Single-phase equivalent circuit of a three-phase induction motor.**

# Induction Motors

- In this circuit, the magnetizing reactance generates a flux that links with both the stator and the rotor and induces a voltage in both circuits.
- The magnetic flux rotates with constant amplitude and synchronous speed.
- This flux cuts the stationary conductors of the stator with the synchronous speed and induces a 60 Hz voltage in the stator windings.
- The rms value of the voltage induced in the stator is:

$$V_{sta} = \frac{N_{sta} \Phi_{max} \omega_{sy}}{\sqrt{2}}$$

# Induction Motors

- The flux rotates with the synchronous speed and the rotor with the motor speed.
- Consequently, the flux cuts the rotor conductors with the speed difference between the rotating flux and the rotor.
- The speed difference is calculated using the slip equation:

$$(\omega_{sy} - \omega_m) = \omega_{sy} s$$

- The induced voltage is:

$$V_{rot} = \frac{N_{rot} \Phi_{max} (\omega_{sy} - \omega_m)}{\sqrt{2}} = \frac{N_{rot} \Phi_{max} \omega_{sy} s}{\sqrt{2}}$$

# Induction Motors

- **The division of the rotor and stator induced voltage results in:**

$$V_{rot} = \frac{N_{rot}}{N_{sta}} V_{sta} s = V_{rot\_s} s$$

- This speed difference determines the frequency of the rotor current

$$f_{rot} = \frac{\omega_{rot}}{2\pi} = \frac{\omega_{sy} - \omega_m}{2\pi} = \frac{\omega_{sy} s}{2\pi} = s f_{sy}$$

- The rotor circuit leakage reactance is:

$$X_{rot\_m} = L_{rot} \omega_{rot} = L_{rot} \omega_{sy} s = X_{rot} s$$

# Induction Motors

- **The relation between rotor current and the rotor-induced voltage is calculated by the loop voltage equation:**

$$\mathbf{V}_{\text{rot}} = \mathbf{V}_{\text{rot}_s} s = \mathbf{I}_{\text{rot}} (R_{\text{rot}} + j X_{\text{rot}} s)$$

- **The division of this equation with the slip yields**

$$\mathbf{V}_{\text{rot}_s} = \mathbf{I}_{\text{rot}} \left( \frac{R_{\text{rot}}}{s} + j X_{\text{rot}} \right)$$

- The implementation of this equation simplifies the equivalent circuit

# Induction Motors


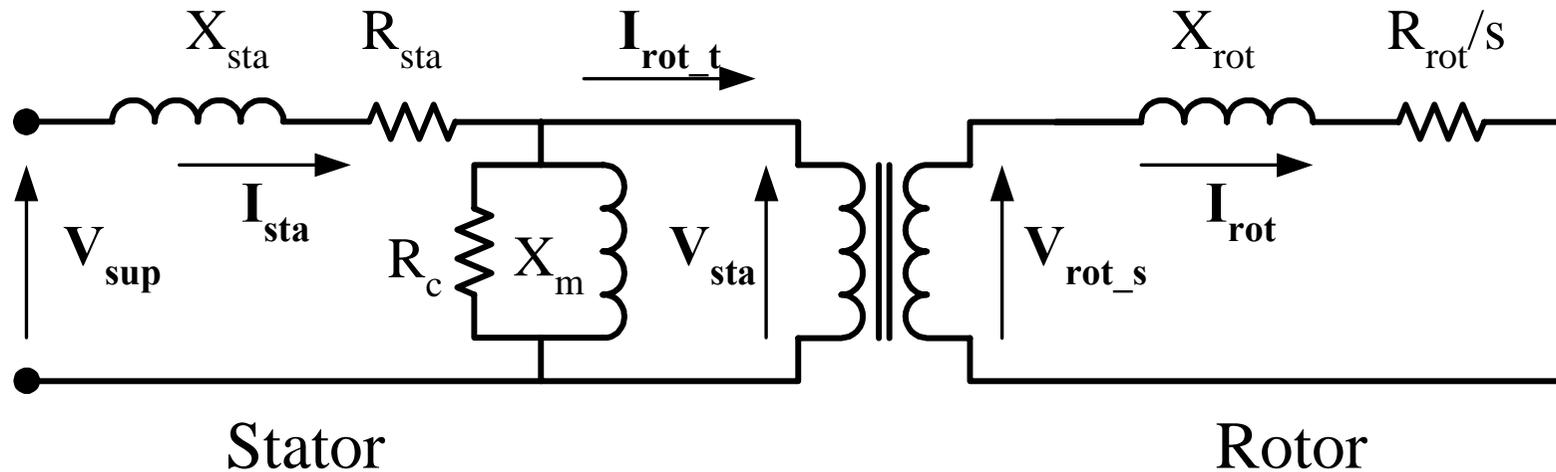


Figure 18 Modified equivalent circuit of a three-phase induction motor.

**The rotor impedance is transferred to the stator side. This eliminates the transformer**

# Induction Motors

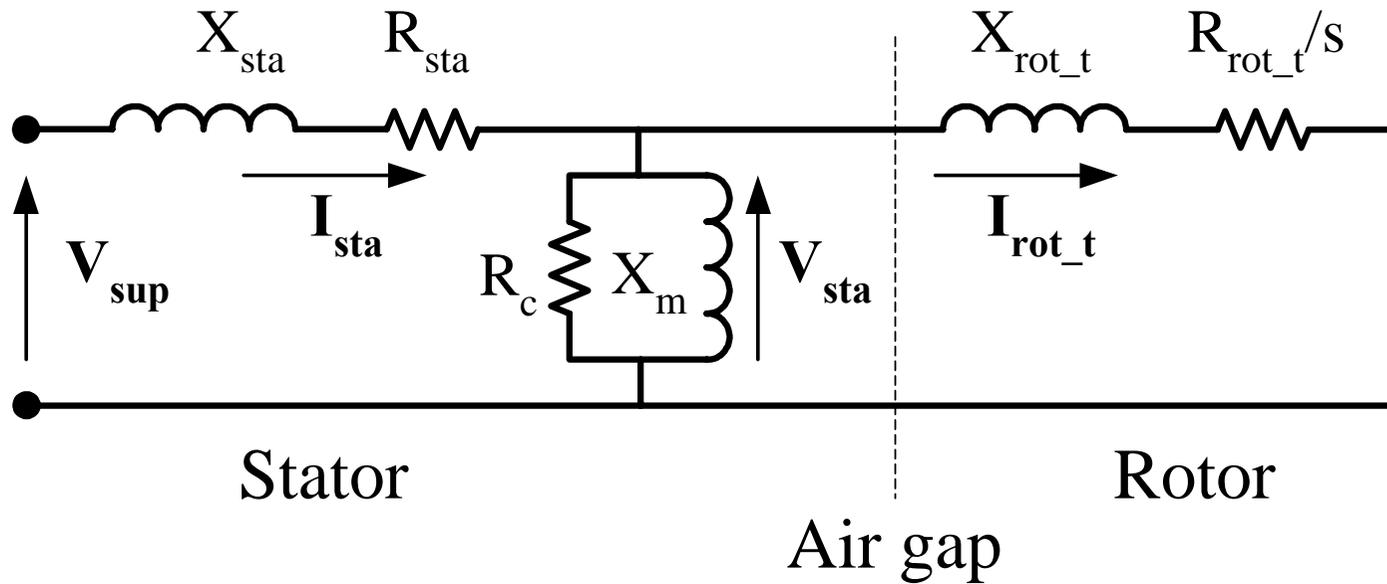

**Figure 19 Simplified equivalent circuit of a three-phase induction motor.**

# Induction Motors


- **The last modification of the equivalent circuit is the separation of the rotor resistance into two parts:**

$$\frac{R_{rot\_t}}{s} = R_{rot\_t} + \frac{[1-s]}{s} R_{rot\_t}$$

- **The obtained resistance represents the outgoing mechanical power**

$$\frac{[1-s]}{s} R_{rot\_t}$$

# Induction Motors

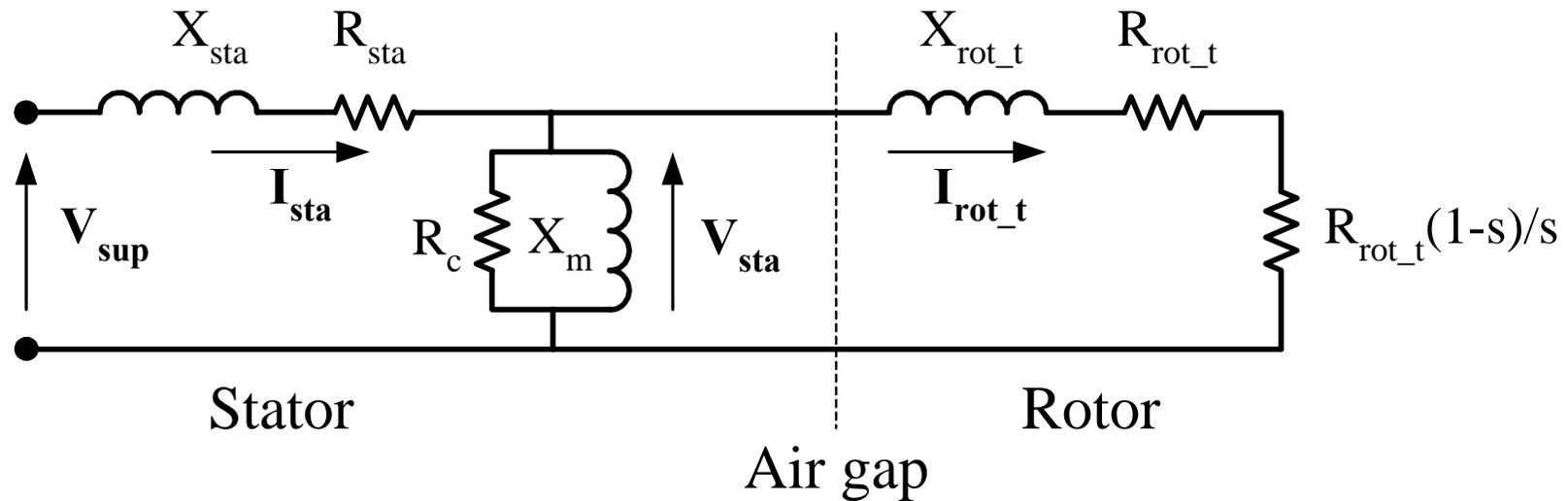

**Figure 20 Final single-phase equivalent circuit of a three-phase induction motor.**

# **Motor performance**

# Induction Motors

- **Figure 21 shows the energy balance in a motor.**
- **The supply power is:**

$$P_{\text{sup}} = \text{Re}(S_{\text{sup}}) = \text{Re}(3 V_{\text{sup}} I_{\text{sta}}^*)$$

- **The power transferred through the air gap by the magnetic coupling is the input power ( $P_{\text{sup}}$ ) minus the stator copper loss and the magnetizing (stator iron) loss.**
- **The electrically developed power ( $P_{\text{dv}}$ ) is the difference between the air gap power ( $P_{\text{ag}}$ ) and rotor copper loss.**

# Induction Motors

- **The electrically developed power can be computed from the power dissipated in the second term of rotor resistance:**

$$P_{dv} = 3 \left| \mathbf{I}_{rot\_t} \right|^2 \left( R_{rot\_t} \frac{1-s}{s} \right)$$

- **The subtraction of the mechanical ventilation and friction losses ( $P_{mloss}$ ) from the developed power gives the mechanical output power**

$$P_{out} = P_{dv} - P_{mloss}$$

# Induction Motors


- **The motor efficiency:**

$$\eta = \frac{P_{\text{out}}}{P_{\text{sup}}}$$

- **Motor torque:**

$$M = \frac{P_{\text{out}}}{\omega_{\text{m}}}$$

# Induction Motors

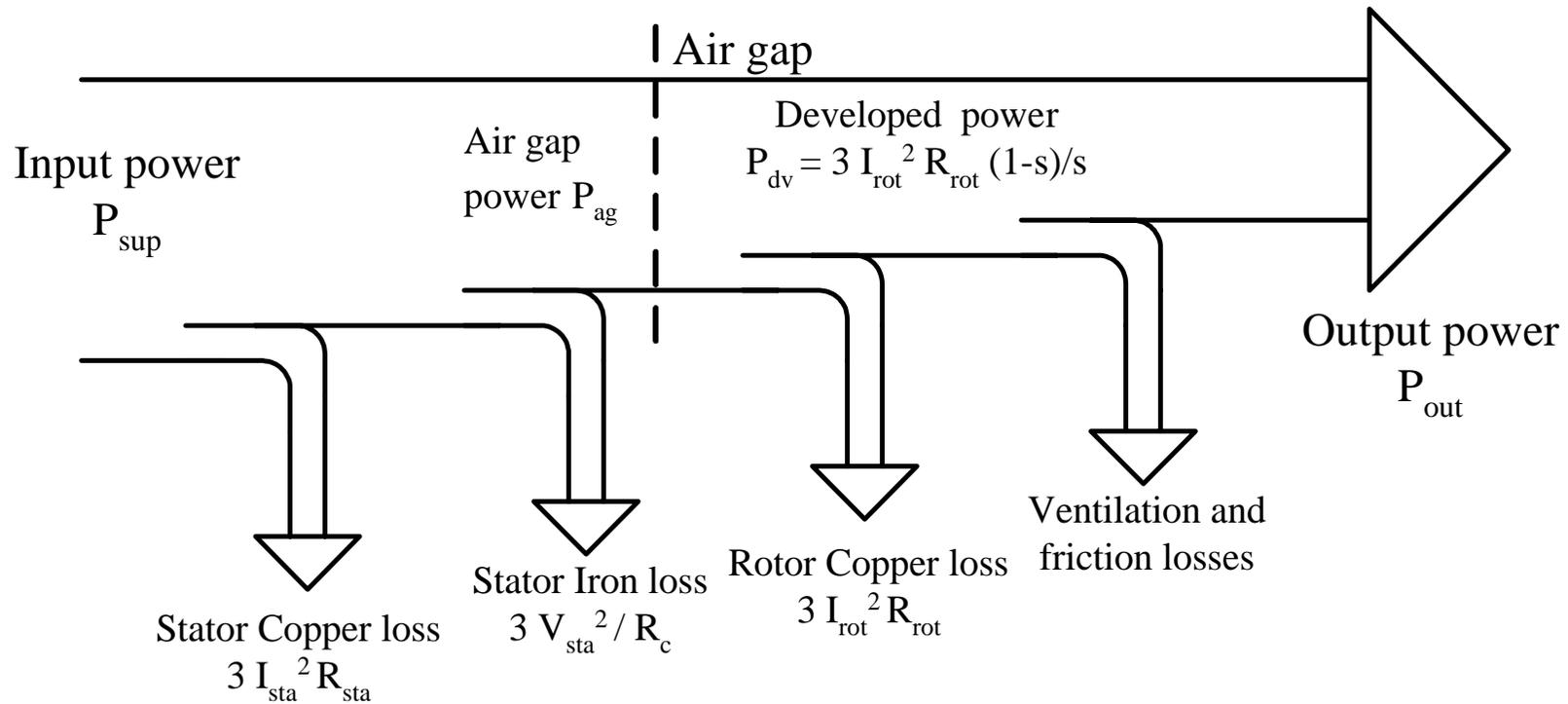

**Figure 21 Motor energy balance flow diagram.**

## **7.3.4 Motor performance analysis**

# Induction Motors


## 1) Motor impedance

$$Z_{\text{rot}_t}(s) := j \cdot X_{\text{rot}_t} + R_{\text{rot}_t} + R_{\text{rot}_t} \cdot \frac{(1-s)}{s}$$

$$Z_m := \frac{j \cdot X_m \cdot R_c}{j \cdot X_m + R_c}$$

$$Z_{\text{sta}} := j \cdot X_{\text{sta}} + R_{\text{sta}}$$

$$Z_{\text{mot}}(s) := Z_{\text{sta}} + \frac{Z_m \cdot Z_{\text{rot}_t}(s)}{Z_m + Z_{\text{rot}_t}(s)}$$

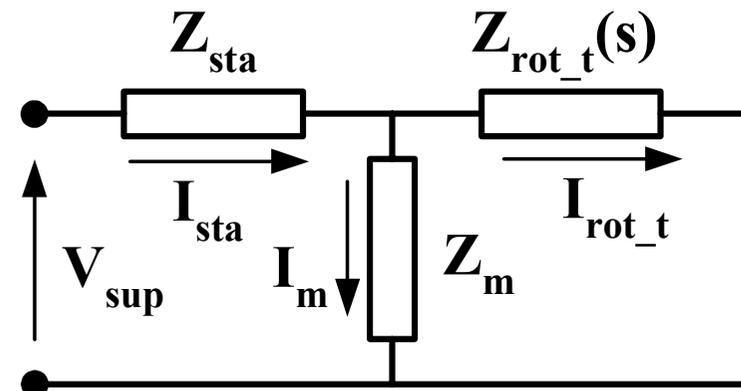

**Figure 7.22 Simplified motor equivalent circuit.**


# Induction Motors

## 2) Motor Current

$$V_{\text{sup}} := \frac{V_{\text{mot}}}{\sqrt{3}}$$

$$I_{\text{sta}}(s) := \frac{V_{\text{sup}}}{Z_{\text{mot}}(s)}$$

$$I_{\text{rot\_t}}(s) := I_{\text{sta}}(s) \cdot \frac{Z_{\text{m}}}{Z_{\text{m}} + Z_{\text{rot\_t}}(s)}$$

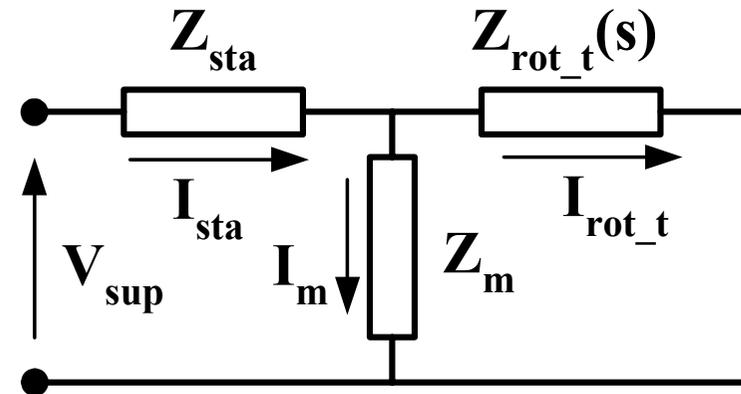

**Figure 7.22 Simplified motor equivalent circuit.**

# Induction Motors

## 3) Motor Input Power


$$S_{\text{sup}}(s) := 3 \cdot V_{\text{sup}} \cdot \overline{I_{\text{sta}}(s)} \quad P_{\text{sup}}(s) := \text{Re}(S_{\text{sup}}(s))$$
$$\text{Pf}_{\text{sup}}(s) := \frac{P_{\text{sup}}(s)}{|S_{\text{sup}}(s)|} \quad Q_{\text{sup}}(s) := \text{Im}(S_{\text{sup}}(s))$$

## 4) Motor Output Power and efficiency

$$P_{\text{dev}}(s) := 3 \cdot \left( |I_{\text{rot\_t}}(s)| \right)^2 \cdot R_{\text{rot\_t}} \cdot \frac{(1-s)}{s}$$
$$P_{\text{mech}}(s) := P_{\text{dev}}(s) - P_{\text{mech\_loss}} \quad \eta(s) := \frac{P_{\text{mech}}(s)}{P_{\text{sup}}(s)}$$

# Induction Motors

$s := 0.1 \cdot \% , 0.2 \% \dots 100 \cdot \%$

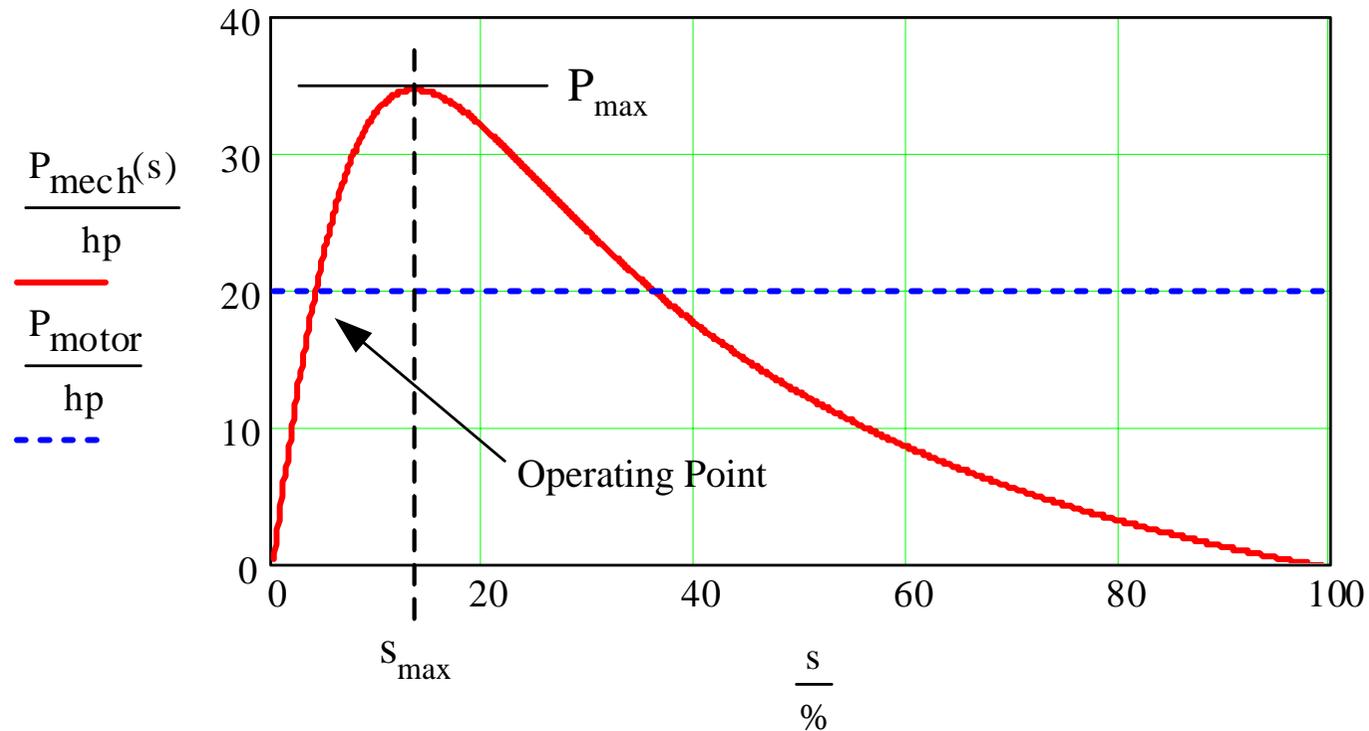

**Figure 24 Mechanical output power versus slip.**

# Induction Motors

## 5. Motor Speed

$$\text{rpm} := \frac{1}{\text{min}}$$

$$n_{\text{sy}} := \frac{f}{\frac{p}{2}}$$

$$n_{\text{m}}(s) := n_{\text{sy}} \cdot (1 - s)$$


$$\omega_{\text{m}}(s) := 2 \cdot \pi \cdot n_{\text{m}}(s)$$

## 6. Motor Torque

$$T_{\text{m}}(s) := \frac{P_{\text{mech}}(s)}{\omega_{\text{m}}(s)}$$

# Induction Motors


$s := 0.5\% , 0.6\% \dots 80\%$

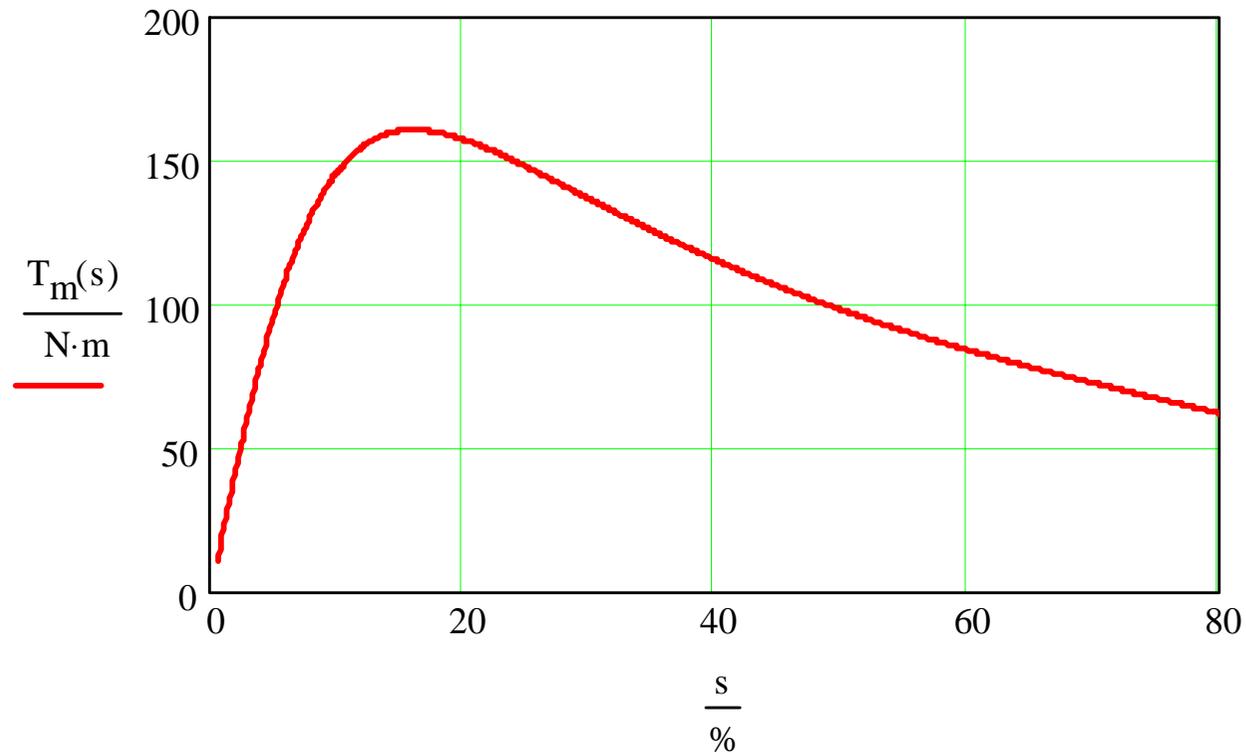

**Figure 25 Torque versus slip.**


# Induction Motors

$s := 0.5\% , 0.6\% \dots 80\%$

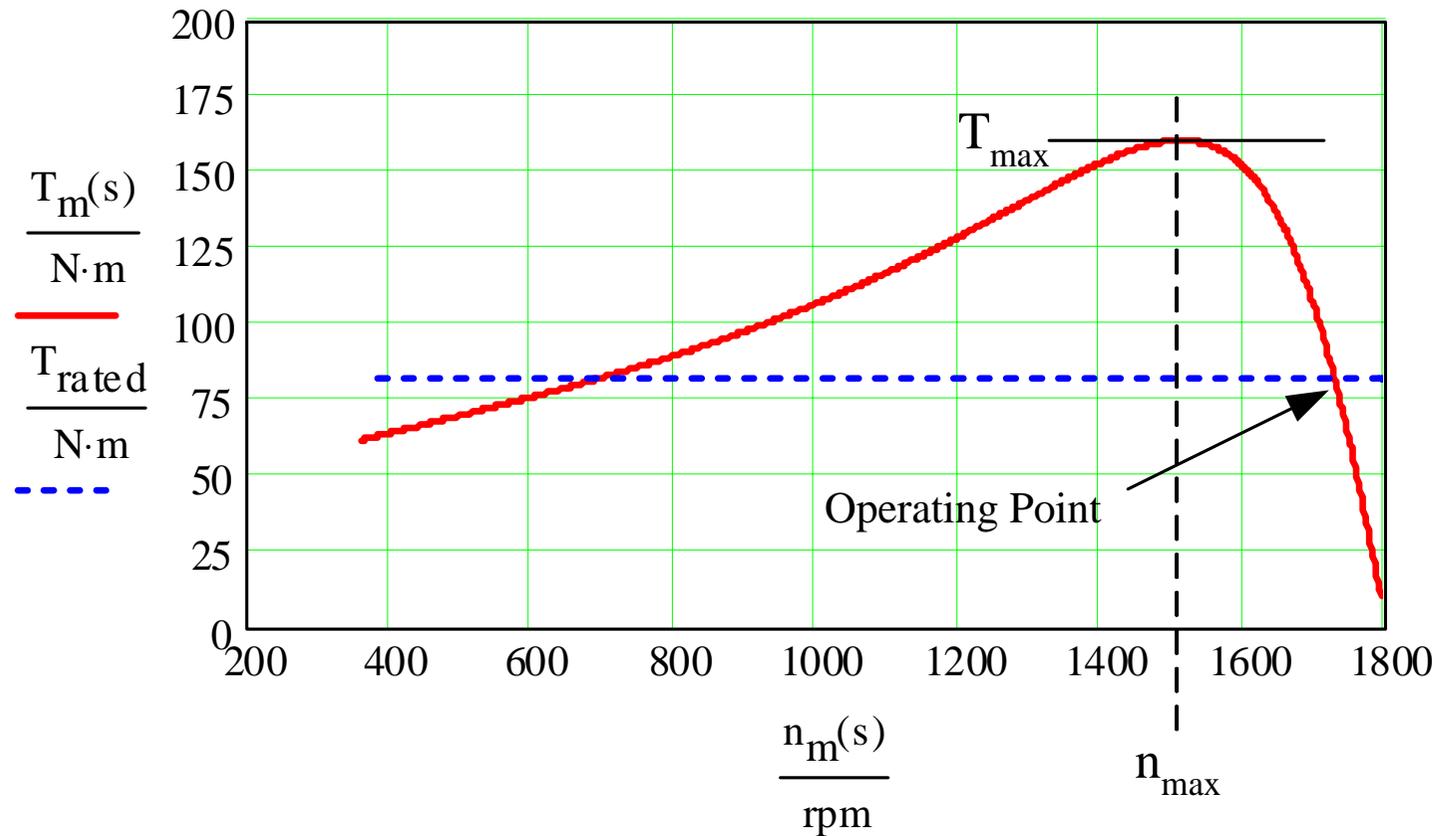

**Figure 26 Torque versus speed.**

# Induction Motors

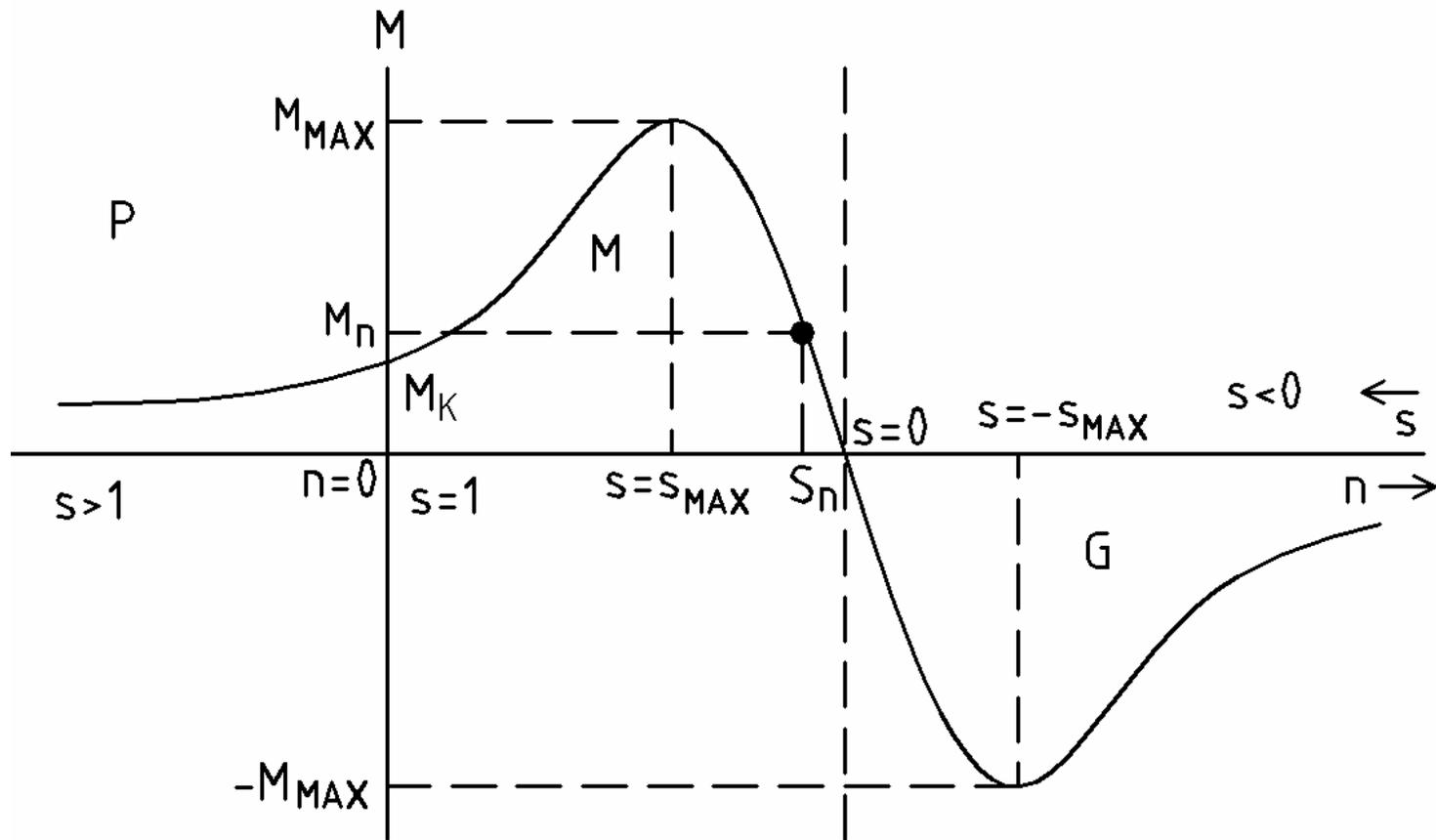

# Induction Motors

## Motor Starting torque

- When the motor starts at  $s = 1$ ,
- The ventilation losses are zero and the friction loss is passive. The negative friction loss does not drive the motor backwards.
- The mechanical losses are zero when  $s = 1$
- This implies that the starting torque is calculated from the developed power instead of the mechanical output power.

# Induction Motors

## Motor Starting torque

$$M_{m\_start}(s) := \frac{3 \cdot \left( |I_{rot\_t}(s)| \right)^2 \cdot R_{rot\_t} \cdot \frac{(1-s)}{s}}{2 \cdot \pi \cdot n_{sy} \cdot (1-s)}$$

$$M_{m\_start}(s) := \frac{3 \cdot \left( |I_{rot\_t}(s)| \right)^2 \cdot \frac{R_{rot\_t}}{s}}{2 \cdot \pi \cdot n_{sy}}$$

# Induction Motors

- **Kloss formula**


$$M = \frac{2 M_{MAX}}{\frac{s_{MAX}}{s} + \frac{s}{s_{MAX}}}$$

# Induction Motors

## Circular diagram

Měřítka proudů:  $m_A \dots \text{A/cm}$   
 Měřítka výkonů:  $m_p = \sqrt{3} U_n \cdot m_A \dots \text{W/cm}$   
 Měřítka momentů:  $m_M = \frac{m_p}{\omega_s} \dots \text{Nm/cm}$

KRUŽNICOVÝ DIAGRAM

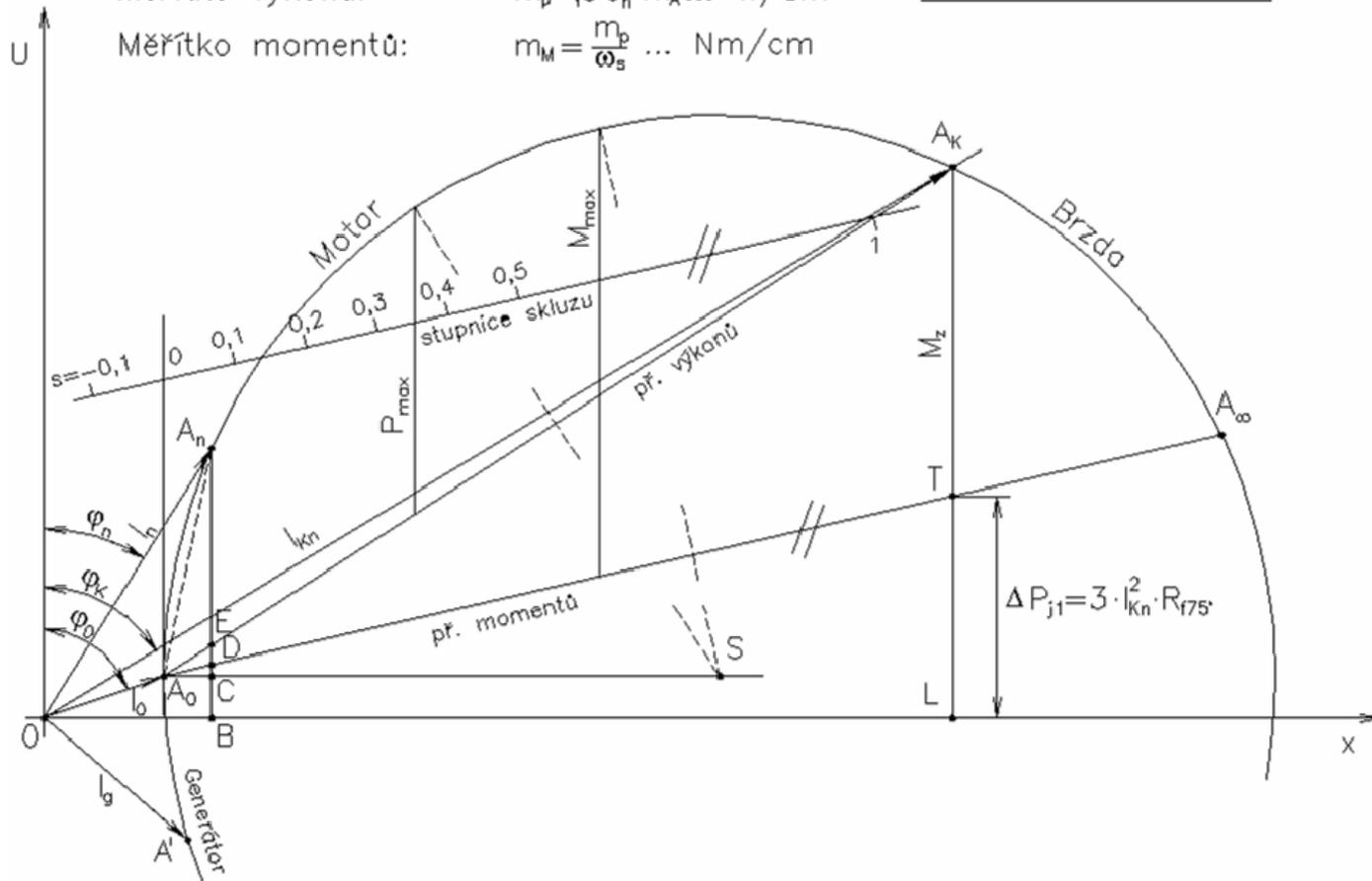

# Induction Motors

- The resistances and reactance in the equivalent circuit for an induction motor can be determined by a series of measurements. The measurements are:
  - No-load test. This test determines the magnetizing reactance and core loss resistance.
  - Blocked-rotor test. This test gives the combined value of the stator and rotor resistance and reactance.
  - Stator resistance measurement.

# Induction Motors


## No-load test

- **The motor shaft is free**
- **The rated voltage supplies the motor.**
- **In the case of a three-phase motor:**
  - **the line-to-line voltages,**
  - **line currents**
  - **three-phase power using two wattmeters are measured**


# Induction Motors

## No-load test

**Fig 29 Equivalent motor circuit in no-load test**

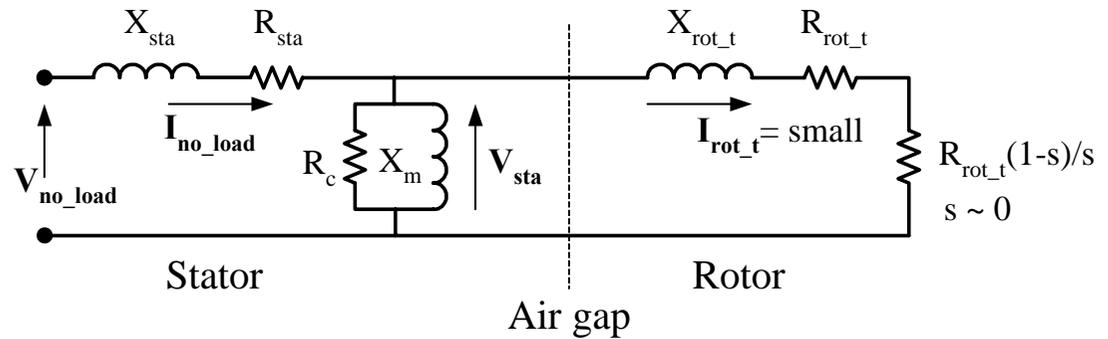

**Fig. 30 Simplified equivalent motor circuit in no-load test**

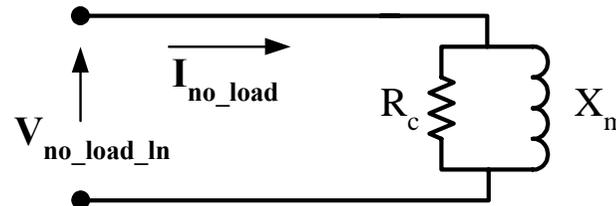

# Induction Motors

## No-load test

$$V_{\text{no\_load\_ln}} := \frac{V_{\text{no\_load}}}{\sqrt{3}}$$

$$R_c := \frac{V_{\text{no\_load\_ln}}^2}{P_{\text{no\_load\_A}}}$$

$$P_{\text{no\_load\_A}} := \frac{P_{\text{no\_load}}}{3}$$

$$S_{\text{no\_load\_A}} := V_{\text{no\_load\_ln}} \cdot I_{\text{no\_load}}$$

$$Q_{\text{no\_load\_A}} := \sqrt{S_{\text{no\_load\_A}}^2 - P_{\text{no\_load\_A}}^2}$$

$$X_m := \frac{V_{\text{no\_load\_ln}}^2}{Q_{\text{no\_load\_A}}}$$

# Induction Motors

## Blocked-rotor test

- The rotor is blocked to prevent rotation
- The supply voltage is reduced until the motor current is around the rated value.
- The motor is supplied by reduced voltage and reduced frequency. The supply frequency is typically 15 Hz.
- In the case of a three-phase motor:
  - the line-to-line voltages,
  - line currents
  - three-phase power using two wattmeters are measured

# Induction Motors

## Blocked-Rotor test

Figure 31 Equivalent motor circuit for blocked-rotor test


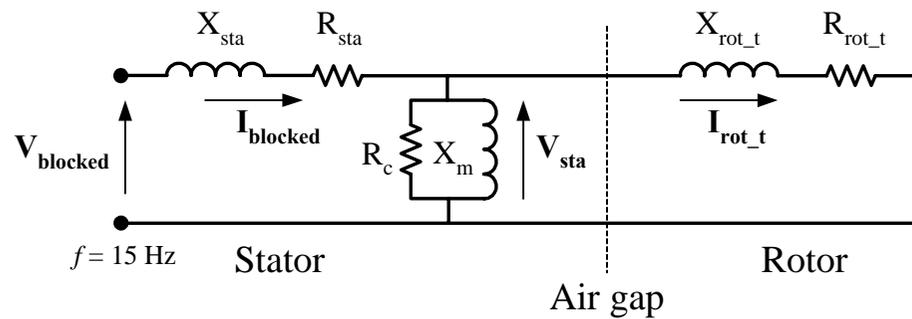


Figure 32 Simplified equivalent motor circuit for blocked-rotor test

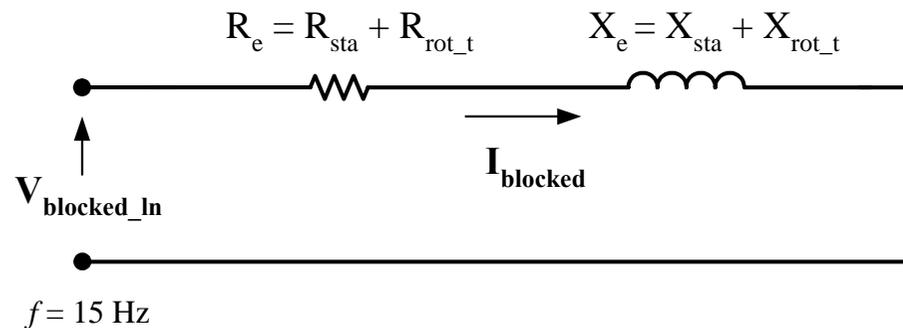

# Induction Motors

## Blocked-Rotor test

$$V_{\text{blocked\_ln}} := \frac{V_{\text{blocked}}}{\sqrt{3}}$$

$$P_{\text{blocked\_A}} := \frac{P_{\text{blocked}}}{3}$$

$$R_e := \frac{P_{\text{blocked\_A}}}{I_{\text{blocked}}^2}$$

The stator resistance was measured directly

$$R_{\text{rot\_t}} := R_e - R_{\text{sta}}$$

# Induction Motors

## Blocked-Rotor test

The magnitude of the motor impedance

$$Z_{\text{blocked}} := \frac{V_{\text{blocked\_ln}}}{I_{\text{blocked}}}$$

The leakage reactance at 15 Hz

$$X_{e\_15\text{Hz}} := \sqrt{Z_{\text{blocked}}^2 - R_e^2}$$

The leakage reactance at 60 Hz

$$X_e := X_{e\_15\text{Hz}} \cdot \frac{60\text{Hz}}{15\text{Hz}}$$

# Numerical Example

# Induction Motors

A three -phase 30hp, 208V, 4 pole, 60Hz, wye connected induction motor was tested, the obtained results are:

**No load test, 60 Hz**

$$V_{nL} := 208V \quad P_{nL} := 1600W \quad I_{nL} := 22A$$

**Blocked Rotor test, 15Hz**

$$V_{br} := 21V \quad P_{br} := 2100W \quad I_{br} := 71A \quad f_{br} := 15Hz$$

**DC test**

$$V_{dc} := 12V \quad I_{dc} := 75A$$

Motor rating:

$$P_{mot\_rated} := 30hp \quad V_{mot\_ll} := 208V \quad pf_{mot} := 0.8$$

$$p := 4$$

$$f := 60Hz$$

**Calculate :**

**a) The equivalent circuit parameters**

**b) Motor rated current and synchronous speed**

**Draw the equivalent circuit**

# Induction Motors

**No load test** , Determine the core losses  $R_c$  and magnetizing reactance  $X_m$

Single phase values:

$$P_{nL\_1F} := \frac{P_{nL}}{3} \quad V_{nL\_ln} := \frac{V_{nL}}{\sqrt{3}}$$

$$R_c := \frac{(V_{nL\_ln})^2}{P_{nL\_1F}}$$

$$R_c = 27.04\Omega$$

$$Y_{nL} := \frac{I_{nL}}{V_{nL\_ln}}$$

$$Y_{nL} = 0.183S$$

$$X_m := i \cdot \frac{1}{\sqrt{Y_{nL}^2 - \left(\frac{1}{R_c}\right)^2}}$$

$$X_m = 5.573i\Omega$$

# Induction Motors

## Block Rotor test,

Neglect the magnetizing branch. Consider only the  $X_{\text{sta}}+X_{\text{rot}}$  and  $R_{\text{sta}}+R_{\text{rot}}$

$$X_{\text{br}} = X_{\text{sta}} + X_{\text{rot}} \quad R_{\text{br}} = R_{\text{sta}} + R_{\text{rot}}$$

Single phase values:

$$P_{\text{br}_1\text{F}} := \frac{P_{\text{br}}}{3} \quad V_{\text{br}_1\text{ln}} := \frac{V_{\text{br}}}{\sqrt{3}}$$

Resistance value is:

$$R_{\text{br}} := \frac{P_{\text{br}_1\text{F}}}{I_{\text{br}}^2} \quad R_{\text{br}} = 0.139\Omega$$

# Induction Motors

$$Z_{br} := \frac{V_{br\_ln}}{I_{br}} \quad Z_{br} = 0.171\Omega$$

$$X_{br\_15Hz} := i \cdot \sqrt{Z_{br}^2 - R_{br}^2} \quad X_{br\_15Hz} = 0.099i\Omega$$

The reactance at 60 Hz is:

$$X_{br\_60Hz} := X_{br\_15Hz} \cdot \frac{60}{15} \quad X_{br\_60Hz} = 0.398i\Omega$$

$$X_{br} := i \cdot \sqrt{(Z_{br}^2 - R_{br}^2)} \cdot \frac{60Hz}{f_{br}} \quad X_{br} = 0.398i\Omega$$

# Induction Motors

Determination of R1 and R2 and X1 and X2

$$X_{\text{sta}} := \frac{X_{\text{br}}}{2}$$

$$X_{\text{rot}} := X_{\text{sta}}$$

$$X_{\text{sta}} = 0.199i\Omega$$

Y connected motor

$$R_{\text{sta}} := \frac{V_{\text{dc}}}{2I_{\text{dc}}}$$

$$R_{\text{rot}} := R_{\text{br}} - R_{\text{sta}}$$


$$R_{\text{sta}} = 0.08\Omega$$

$$R_{\text{rot}} = 0.059\Omega$$

# Induction Motors

## a) The equivalent circuit parameters

### a) The equivalent circuit parameters

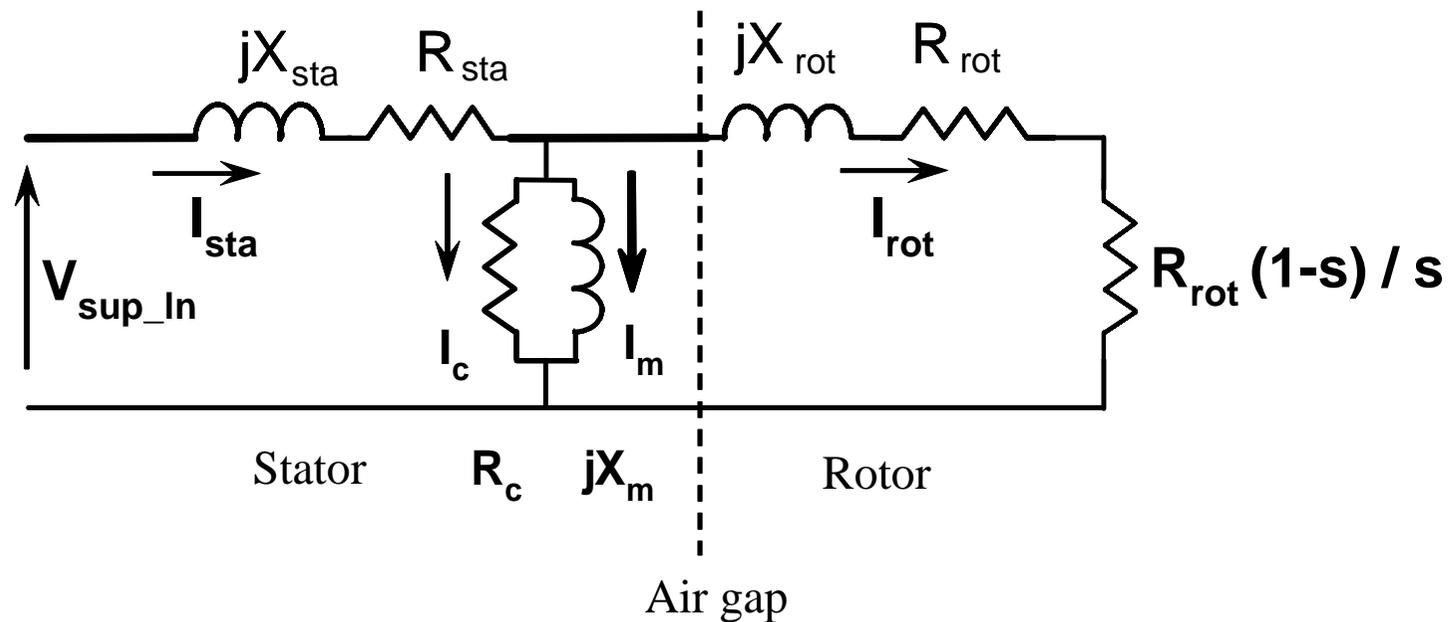

# Induction Motors

## C) Motor rated current and synchronous speed

$$S_{\text{rated}} := \frac{P_{\text{mot\_rated}}}{\text{pf}_{\text{mot}}}$$

$$S_{\text{rated}} = 27.964 \text{ kV} \cdot \text{A}$$

$$I_{\text{mot\_rated}} := \frac{S_{\text{rated}}}{\sqrt{3} \cdot V_{\text{mot\_ll}}}$$

$$I_{\text{mot\_rated}} = 77.62 \text{ A}$$

$$\text{rpm} := \frac{1}{\text{min}}$$

$$n_{\text{synch}} := \frac{f}{\frac{p}{2}}$$

$$n_{\text{synch}} = 30 \text{ Hz}$$

$$n_{\text{synch}} = 1800 \text{ rpm}$$